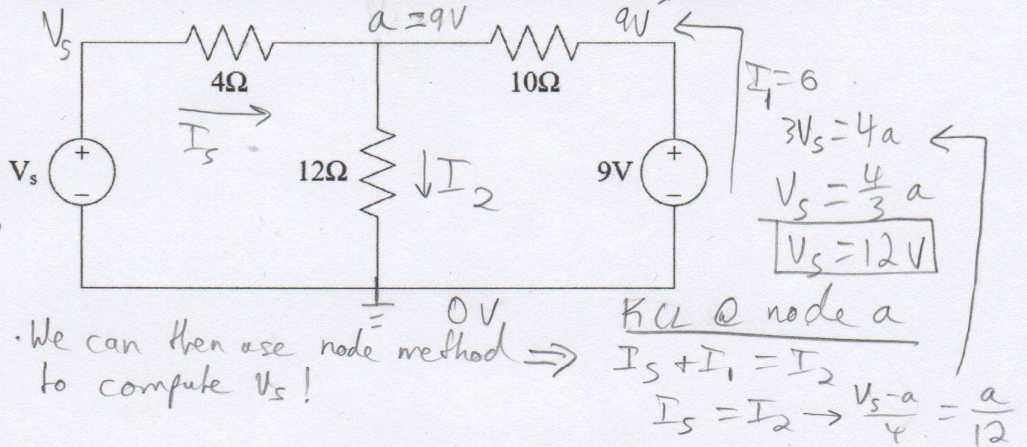



1. Find the value of the voltage source V_s such that the 9V source neither absorbs nor supplies power.

- If the 9V source neither absorbs nor supplies power, $P=0$, and thus its current must be zero!
- By Ohm's Law, we know the 10Ω resistor must then have no voltage drop. Thus, $a=9V$.



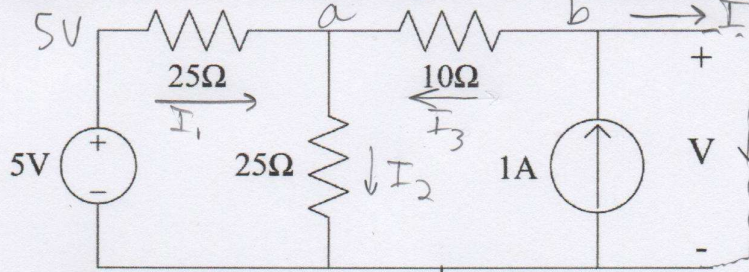2. Obtain the Thevenin and Norton Equivalents for the following circuit. That is, find V_T , I_N , and R_T .

- Finding V_{oc}
- Want to find node voltage b .
 - First, let's find a .
- KCL @ node a



All three values agree by Ohm's Law!

$$I_1 + I_3 = I_2$$

$$\frac{5-a}{25} + 1 = \frac{a}{25}$$

$$a = 15V \rightarrow I_3 = 1 = \frac{b-a}{10}$$

$$\rightarrow b = V_{oc} = 25V$$

Finding I_{sc}

$b=0$ now

Let's find node a

KCL @ node a

$$I_1 + I_3 = I_2 \rightarrow a = \frac{10}{9}$$

$$\frac{5-a}{25} + \frac{0-a}{10} = \frac{a}{25}$$

$$I_{sc} = \frac{10}{9}$$

Finding R_{eff}


Source Suppression

$$R_{eff} = (25 \parallel 25) + 10$$

$$R_{eff} = 22.5\Omega$$

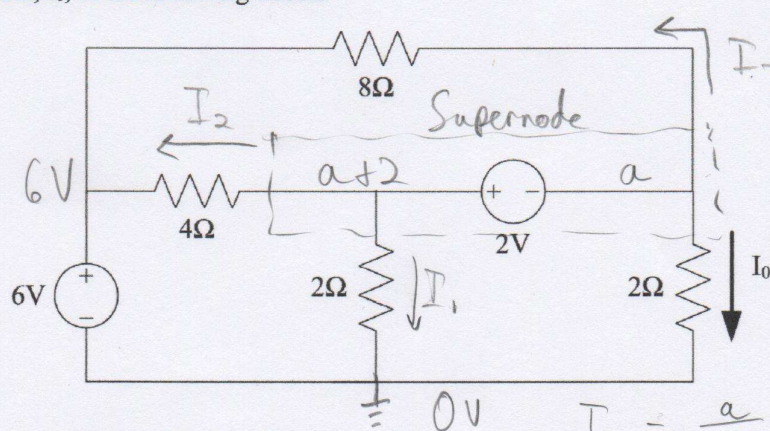3. Find the labeled current, I_o , in the following circuit.

- Finding node a will make finding I_o trivial.
- We will place a supernode around the 2V source because it is a floating source!



KCL @ Supernode

$$I_o + I_1 + I_2 + I_3 = 0$$

$$\frac{a}{2} + \frac{a+2}{2} + \frac{(a+2)-6}{4} + \frac{a-6}{8} = 0 \rightarrow 4a + 4a + 8 + 2a - 8 + a - 6 = 0$$


$$11a = 6 \rightarrow a = \frac{6}{11}V$$

$$I_o = \frac{a}{2}$$

$$I_o = \frac{3}{11}A$$

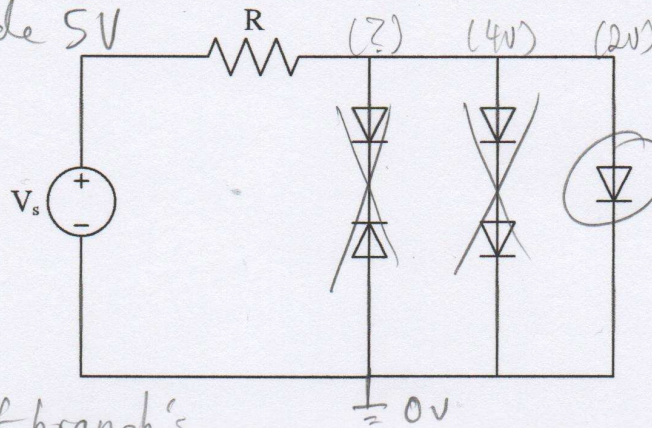4. In the following circuit, $V_s = 5V$ and the V_{ON} for the diodes is $2V$. Determine how many diodes are on.

• Only far right diode is on because the middle branch needs $2 \cdot V_{ON} = 4V$, while the right branch restricts the shared parallel voltage to $2V$.






1 Diode

• Furthermore, the left branch's diodes cannot be on since they point in opposite directions!

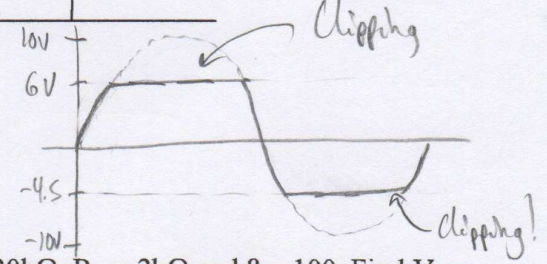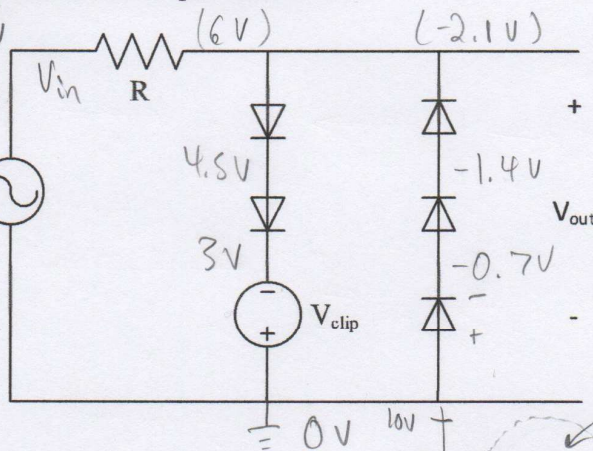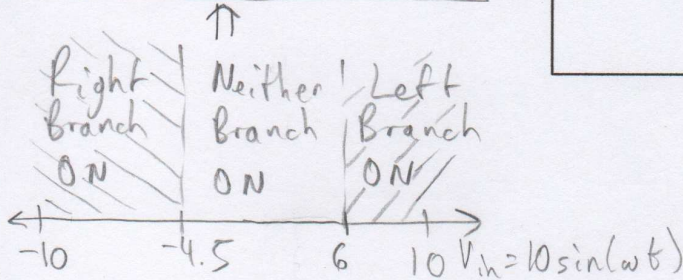5. In the following circuit, $V_{clip} = -3V$ and the V_{ON} for the diodes is $1.5V$. Determine the minimum and maximum values of the output voltage, V_{out} , and sketch the output waveform.

$V_{out} = \begin{cases} 6V, & \text{if left branch ON} \\ V_{in}, & \text{if neither branch ON} \\ -4.5V, & \text{if right branch ON} \end{cases}$
 $10\sin(\omega t)$

$\therefore V_{max} = 6V, V_{min} = -4.5V$



6. For the following circuit, $V_{BE,ON} = 0.4V$, $V_{CE,SAT} = 0.2V$, $R_B = 20k\Omega$, $R_C = 2k\Omega$ and $\beta = 100$. Find V_{CE} for the following input voltages.

a) $V_{in} < V_{BE,ON}$
 \rightarrow Off!
 $V_{CE} = V_{CC} = 10V$

- $V_{in} = 0.3V$
- $V_{in} = 1.0V$
- $V_{in} = 1.4V$

d. What is the smallest value of V_{in} that puts the transistor into saturation?

b) $I_B = \frac{V_{in} - V_{BE,ON}}{R_B} = 30\mu A$ c) $I_B = \frac{V_{in} - V_{BE,ON}}{R_B} = 50\mu A$

$I_C = \beta I_B = 3mA$

$V_{CE} = V_{CC} - I_C R_C = 4V$


$V_{CE} = 4V$

$I_C = \beta I_B = 5mA$

$V_{CE} = V_{CC} - I_C R_C = 0!$

• Not possible to have

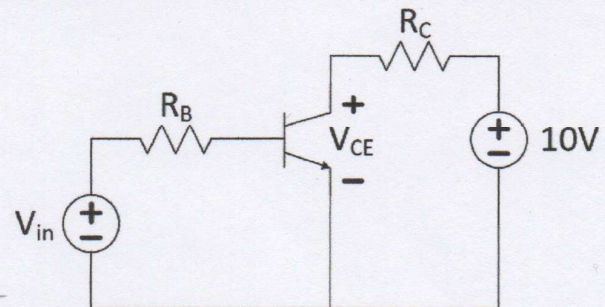$V_{CE} < V_{CE,SAT}$, must be in saturation $\rightarrow V_{CE} = 0.2V$



d) • We can use both active and sat. assumptions: $I_C = \frac{V_{CC} - V_{CE,SAT}}{R_C} = 4.9mA$
 $I_B = \frac{I_C}{\beta} = 49\mu A$
 $V_{in} = I_B R_B + V_{BE,ON}$

$V_{in} = 1.38V$