

ECE 110 Exam 1 Review Session Worksheet


1. Given that $V_1 = -9V$, $V_3 = 5V$, $V_4 = -6V$ and $I_2 = -2A$, $I_3 = 5A$, $I_6 = -7A$, find the remaining unknown voltages and currents, and power for each component. Be careful of signs!

KVL @ Loop 1
 $\sum V_{rises} = \sum V_{drops}$
 $V_1 + V_3 + V_6 = 0$
 $V_6 = -(V_1) - (V_3) = 9 - 5 = 4V$
 $V_6 = 3V$

KVL @ Loop 2
 $\sum V_{rises} = \sum V_{drops}$
 $V_3 + V_2 = V_4$
 $V_2 = V_4 - V_3 = -6 - 5 = -11V$
 $V_2 = -11V$

KVL @ Loop 3
 $\sum V_{rises} = \sum V_{drops}$
 $V_1 + V_5 = V_2$
 $V_5 = V_2 - V_1$
 $= -11 + 9$
 $V_5 = -2V$

Sums to zero!

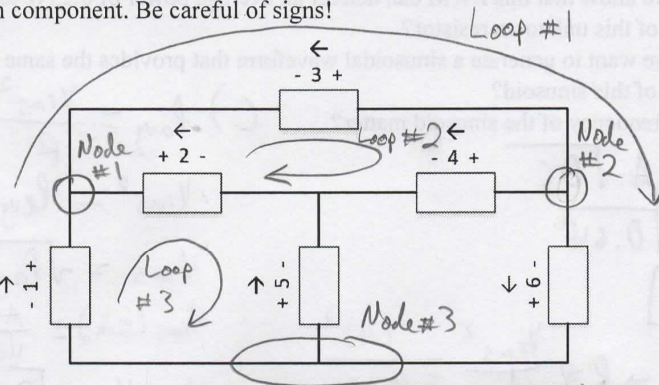

Component	V	I	Standard vs. Non-stand.	P
#1	-9	-3	NS	-27
#2	-11	-2	NS	-22
#3	5	5	S	25
#4	-6	2	S	-12
#5	-2	-4	S	8
#6	4	-7	NS	28

KCL @ Node 1
 $\sum I_{in} = \sum I_{out}$
 $I_1 + I_2 + I_3 = 0$
 $I_1 = -I_2 - I_3 = 2 - 5$
 $I_1 = -3A$


KCL @ Node 2
 $\sum I_{in} = \sum I_{out}$
 $0 = I_3 + I_4 + I_6$
 $I_4 = -I_3 - I_6 = -5 + 7$
 $I_4 = 2A$

KCL @ Node 3
 $\sum I_{in} = \sum I_{out}$
 $I_6 = I_1 + I_5$
 $I_5 = I_6 - I_1 = -7 + 3$
 $I_5 = -4A$

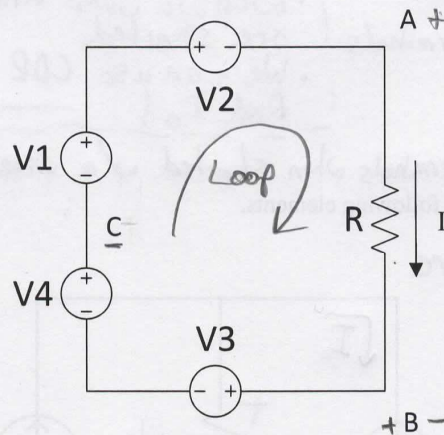2. Given that $V_1 = 1V$, $V_2 = -6V$, $V_3 = 7V$, $V_4 = -2V$, and $R = 10\Omega$, determine V_{AB} , V_{BC} , and I .

V_{AB} = "Voltage from A down to B" = "+" @ A, "-" @ B

V_{AB}
KVL @ Loop:
 $\sum V_{rises} = \sum V_{drops}$
 $V_4 + V_1 = V_2 + V_{AB} + V_3$
 $V_{AB} = V_4 + V_1 - V_2 - V_3$
 $V_{AB} = -2 + 1 + 6 - 7$
 $V_{AB} = -2$



$I = \frac{V_{AB}}{R}$
 $I = -0.2A$

V_{BC}
KVL @ Loop:
 $\sum V_{rises} = \sum V_{drops}$
 $V_1 = V_2 + V_{AB} + V_{BC}$
 $V_{BC} = V_1 - V_2 - V_{AB}$
 $V_{BC} = 1 + 6 + 2$
 $V_{BC} = 9V$

3. Consider a PWM waveform with duty cycle = 64%, peak-to-peak voltage = 5V, and frequency = 20kHz.
- What is the V_{rms} of this PWM waveform?
 - Suppose we know that this PWM can deliver an average power of 0.25W to an unknown resistor. What is the resistance of this unknown resistor?
 - Suppose we want to generate a sinusoidal waveform that provides the same average. What should be the amplitude of this sinusoid?
 - Does the frequency of the sinusoid matter?

a) $V_{rms}(PWM) = A \sqrt{DC}$

$V_{rms} = (5V) \sqrt{0.64}$

$V_{rms} = 4V$

b) $P_{avg} = \frac{V_{rms}^2}{R} \rightarrow R = \frac{V_{rms}^2}{P} = \frac{(4)^2}{0.25}$
 $R = 64\Omega$

c) $P_{avg} = \frac{V_{rms}^2}{R}$

$V_{rms}^2 = P_{avg} R$

$V_{rms} = \sqrt{P_{avg} R}$

$V_{rms}(sch) = \frac{A}{\sqrt{2}}$

$A = V_{rms} \sqrt{2}$

$A = \sqrt{P_{avg} R} \cdot \sqrt{2}$


$A = \sqrt{2 P_{avg} R}$

$A = \sqrt{2 \left(\frac{1}{4}\right) (64)}$

$A = 4\sqrt{2}$

d) Nope!

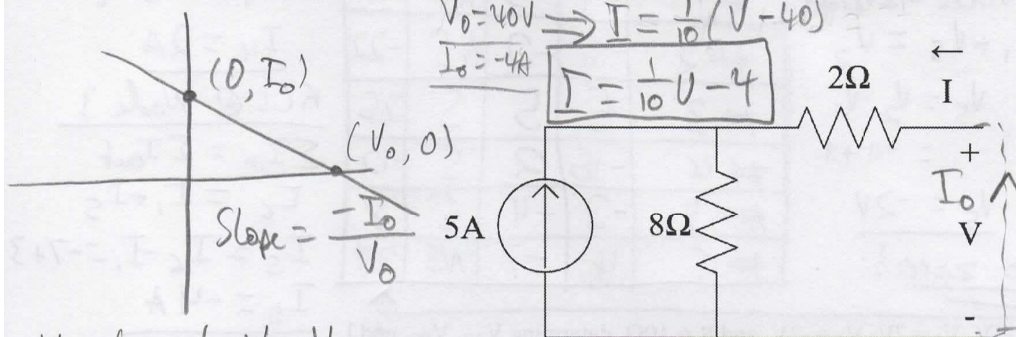4. Find the I-V Characteristic of the following circuit. Be careful of the direction of I!



Finding V_0 :

$I = 0$

∴ There is no voltage drop across 2Ω resistor!

All the current will flow through the 8Ω resistor, which is now in parallel with V.

$V_0 = (5A)(8\Omega) = 40V$

$I_0 = (5) \left(\frac{8}{8+2} \right) (-1) = -4A$

Flip value to match direction of I!

X-intercept: $V = V_0$

$I = 0$

V_0 (voltage across terminals when left open).

y-intercept: $V = 0$

$I = I_0$

Current between terminals when shorted w/ a wire.

Finding I_0 :

• 8Ω || 2Ω when terminals are shorted

• We can use CDR to find I_0 !

5. Compute the power of each of the following elements.

• All three components are in parallel.
 ∴ They must share same voltage


$P_R = \frac{V^2}{R} = \frac{(8)^2}{4}$

$P_R = 16W$

Non-standard current!

$P_I = -IV = -(-3)(8)$

$P_I = 24W$

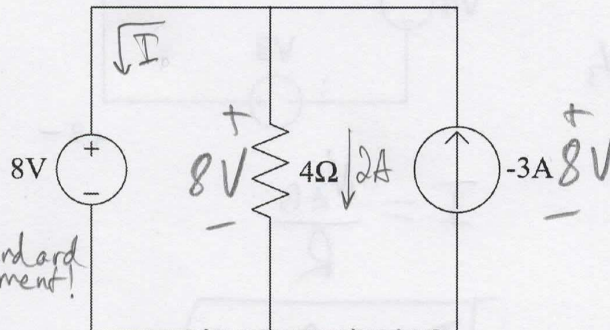

Finding P_I

Method 1:

• Find current for source via KCL

$I + 2A = -3A$

$I = -5A$

$P_I = IV = -40W$

Method 2:

$\sum P = 0$

$\therefore P_V + P_I + P_R = 0$

$P_V = -P_I - P_R = -16 - 24 = -40W \rightarrow P_V = -40W$