


ECE 210 Midterm 1

Presented by Eta Kappa Nu

Complex Numbers


Operation	Rectangular Form	Polar
Addition	Component-wise	Convert to rectangular
Subtraction	Component-wise	Convert to rectangular
Multiplication	FOIL	Magnitudes multiply, angles add
Division	Complex conjugates	Convert to multiplication
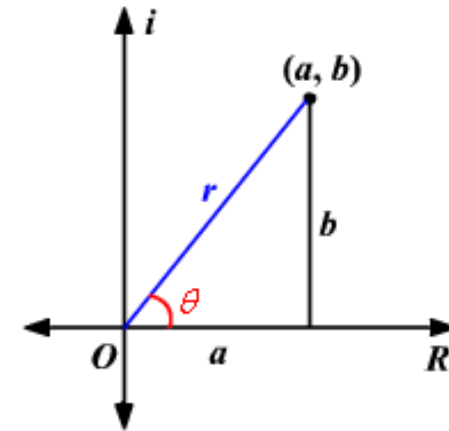
$$e^{j\theta} = \cos(\theta) + j\sin(\theta)$$



Sign Convention


Circuit Element	Voltage-Current Law
Resistor	$v = iR$
Capacitor	$i = C \frac{dv}{dt}$
Inductor	$v = L \frac{di}{dt}$

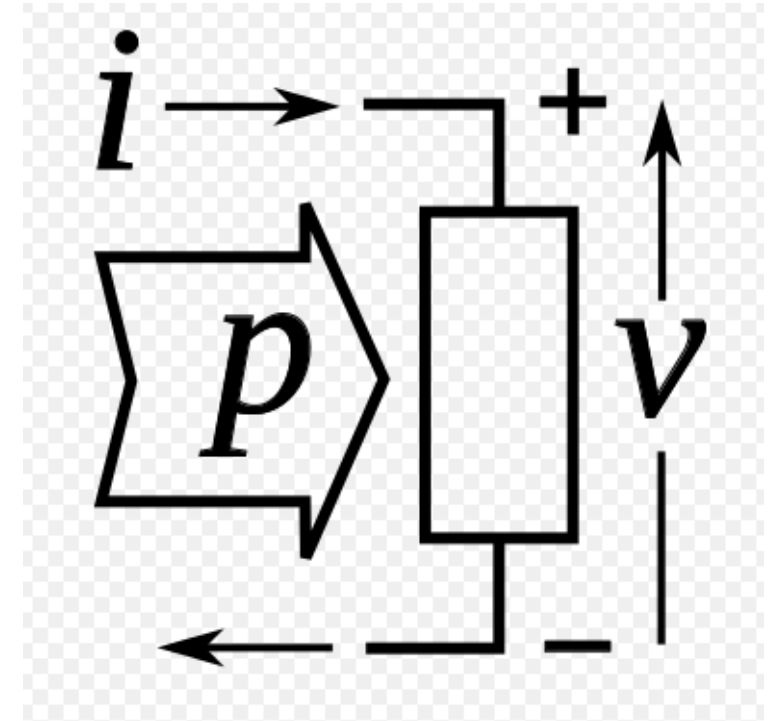

Resistor Combinations


$$R_{eq} = R_1 + R_2 + \dots + R_n$$

Can remove nodes

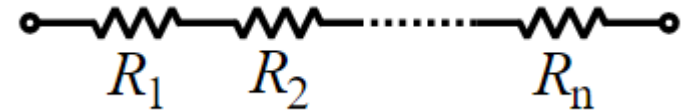


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Can remove loops

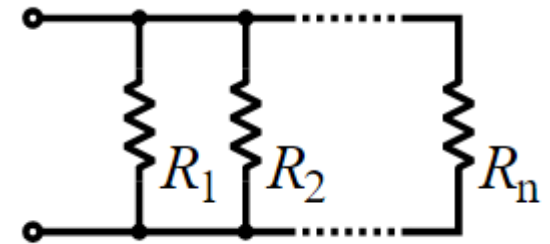


Source Combinations

$$I_{out} = I_1 + I_2 + \cdots + I_n$$

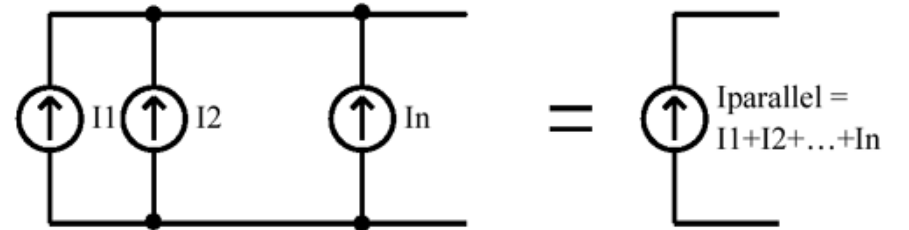

$$V_{out} = V_1 + V_2 + \cdots + V_n$$

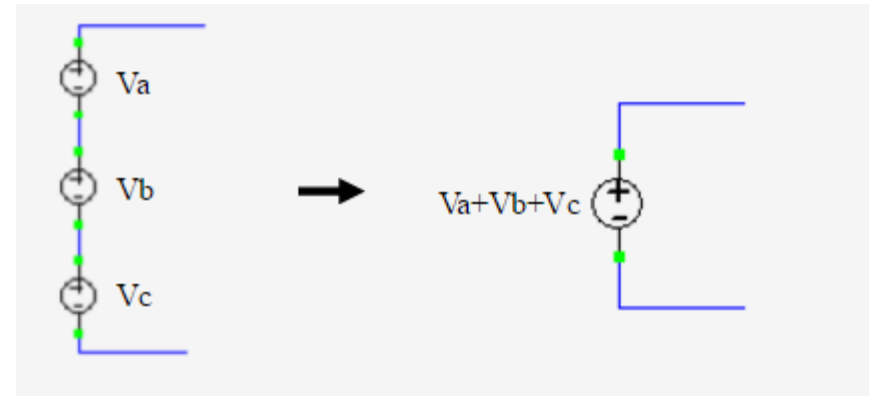

Node Voltage & Loop Current

Node Voltage

- Use KCL at each node
- Use supernodes to consolidate nodes separated by voltage sources

Loop Current

- Use KVL on each loop
- Try to select loops such only one loop goes through a current source

In the end, pick the method with easier equations to solve.

Node Voltage & Loop Current

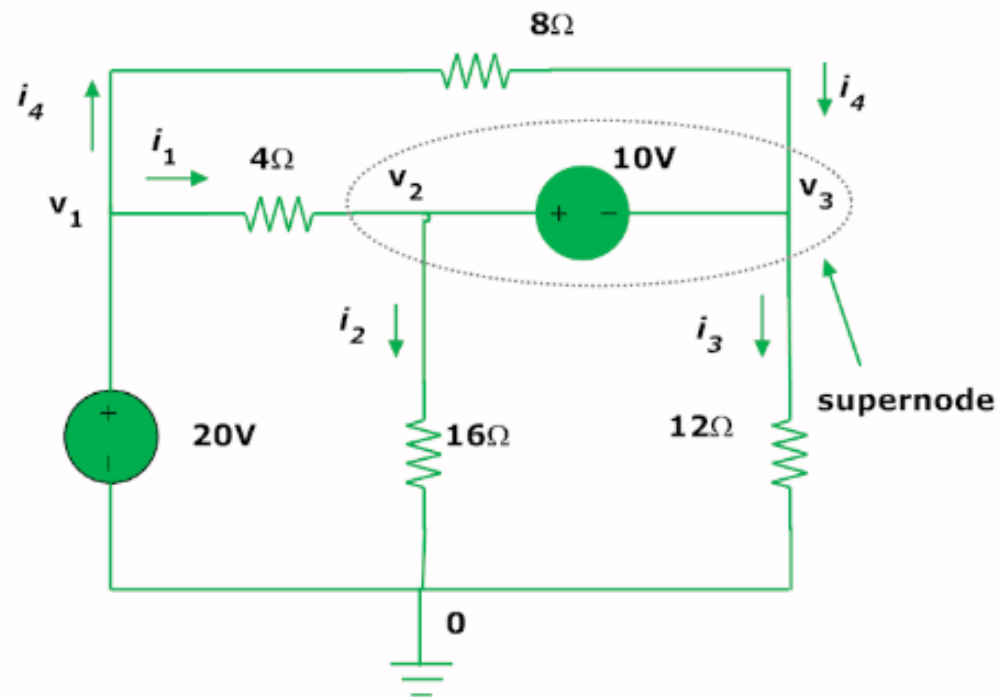


Figure 2


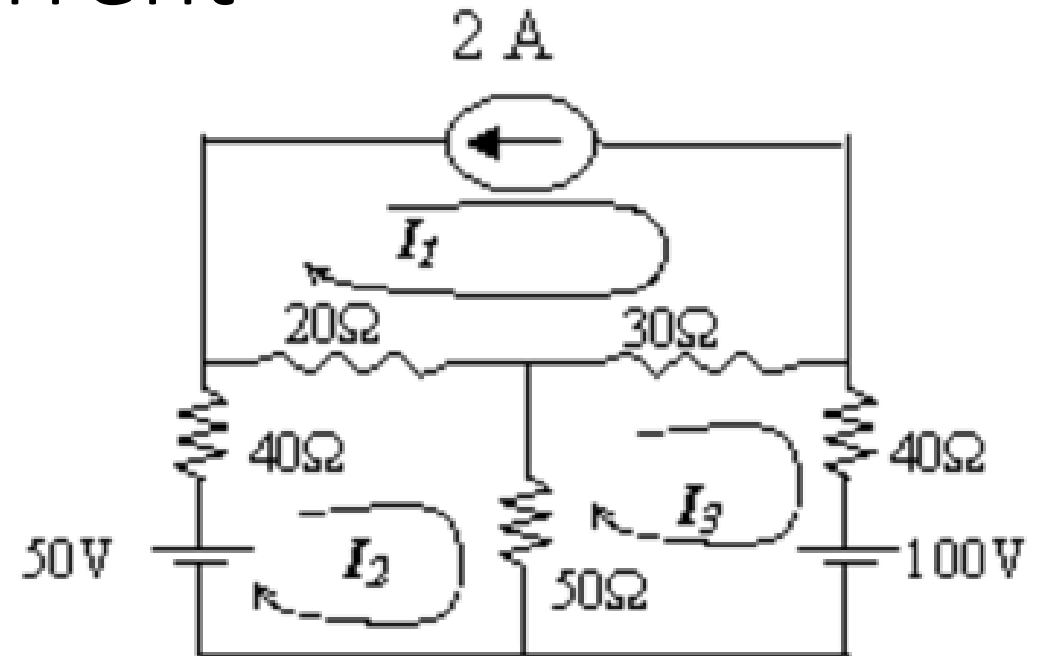


fig. 2.5

In the end, pick the method with easier equations to solve.

Superposition

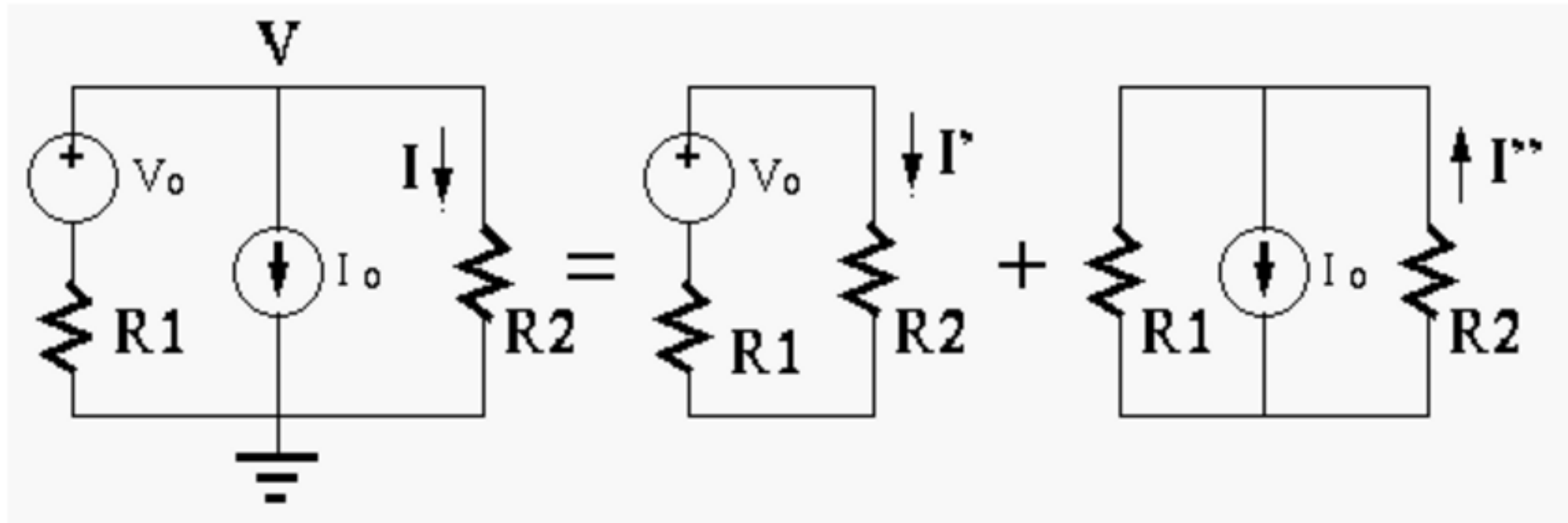

In the end, pick the method with easier equations to solve.


Thevenin Norton Equivalents

V_{TH} is open circuit voltage

I_N is closed circuit current

- If only independent sources, suppress sources and find R_{eq}
- If exist dependent sources, suppress independent sources and use 1 A test current


Thevenin

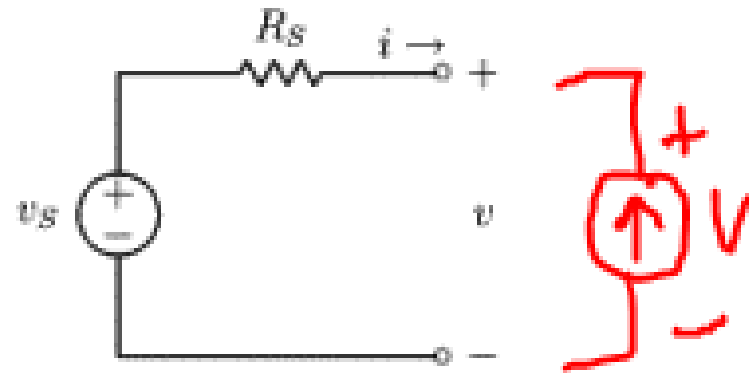

$$v = -R_S i + v_S$$

$$i = \frac{-1}{R_S} v + \frac{v_S}{R_S}$$


Norton

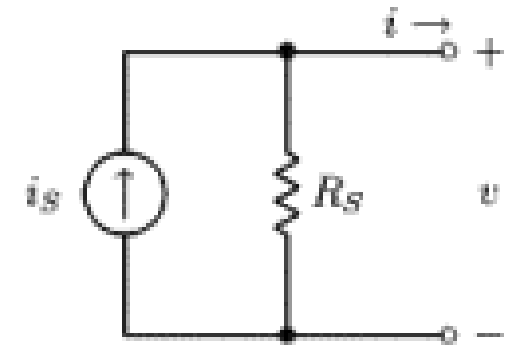

$$v = -R_S i + R_S i_S$$

$$i = \frac{-1}{R_S} v + i_S$$

Maximum power of circuit

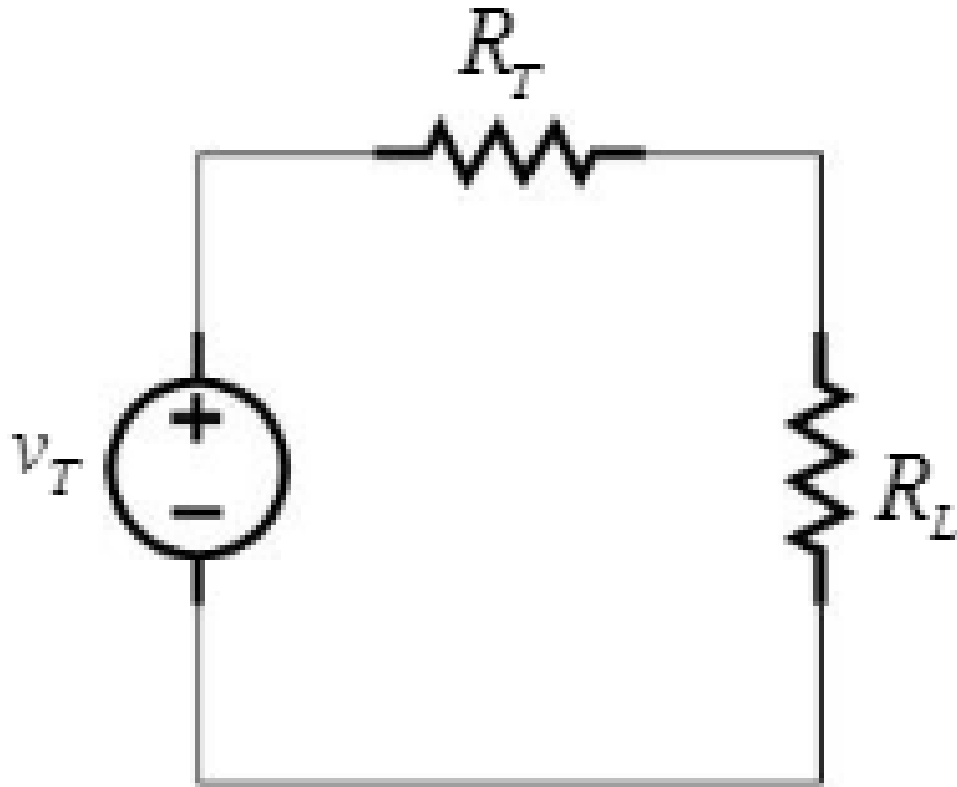


Set $R_L = R_T$

Op Amps

$$v_- = v_+$$

$$i_+ = 0$$

$$i_- = 0$$

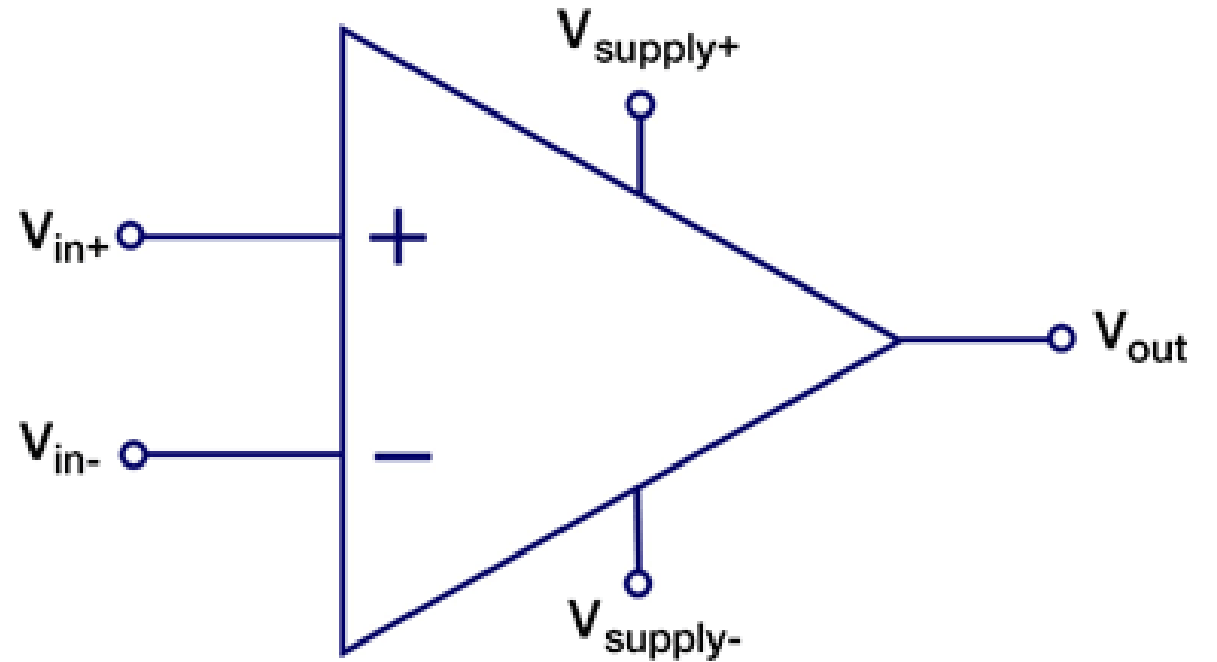

First Order Differential Equations

Given equation, where α and β are constants

$$\frac{dy}{dt} + \alpha y(t) = \beta$$

Then, $y(t) = A + Be^{-\alpha t}$, where A and B are also constants

Get A by finding the limit as $t \rightarrow \infty$, and B from initial conditions

The limit $t \rightarrow \infty$ is the steady state

Time constant: $\tau = \frac{1}{\alpha}$

1. Homogeneous solution – the exponential term
2. Particular solution – the constant

First Order Circuits


- Zero State Response: Solution to ODE when initial state is 0
- Zero Input Response: Solution to ODE when input is 0

$$y(t) = y_h(t) + y_p(t) = y_{ZSR}(t) + y_{ZIR}(t)$$


- At the steady state,
 - Capacitors act as open circuits
 - Inductors act as wires
- Discontinuous functions of time:
 - Voltage across a capacitor
 - Current through an inductor

Practice Problems (from last year's HW)!


3. Find i_x using nodal analysis

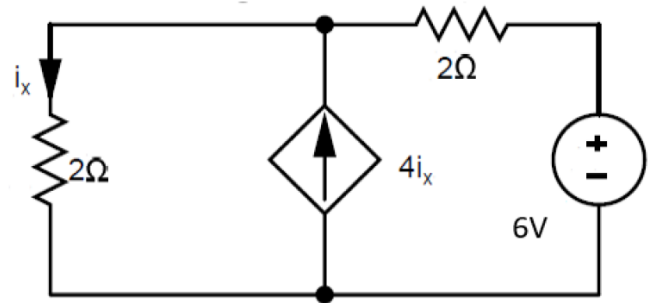

4. Find i_x using loop analysis.

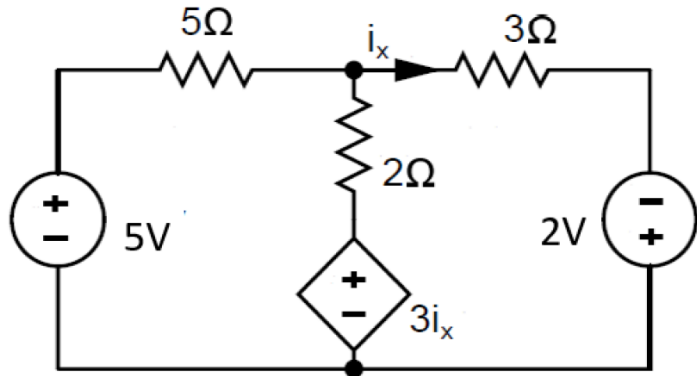


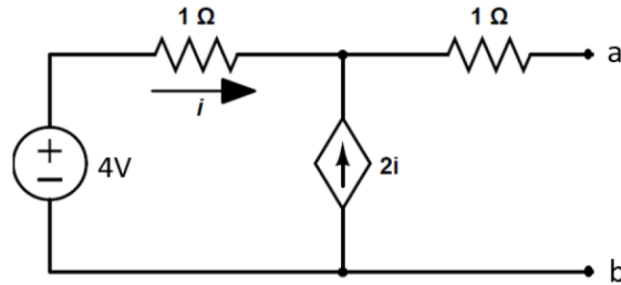5. In the following circuit, find the open-circuit voltage and the short-circuit current between nodes a and b :




Op-Amps!

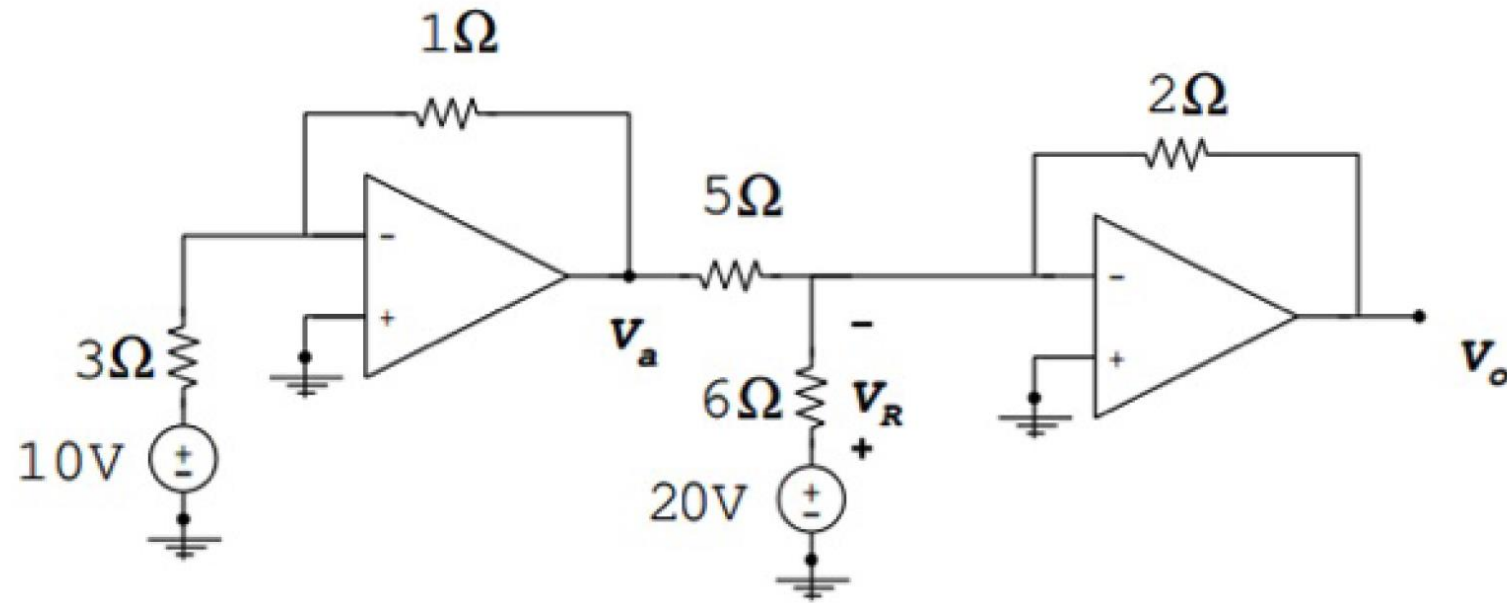5. In the op-amp circuit shown below, determine the voltage V_a , V_R , V_o . Assume the circuit behaves linearly and make use of the ideal op-amp approximation.



RLC with DC sources

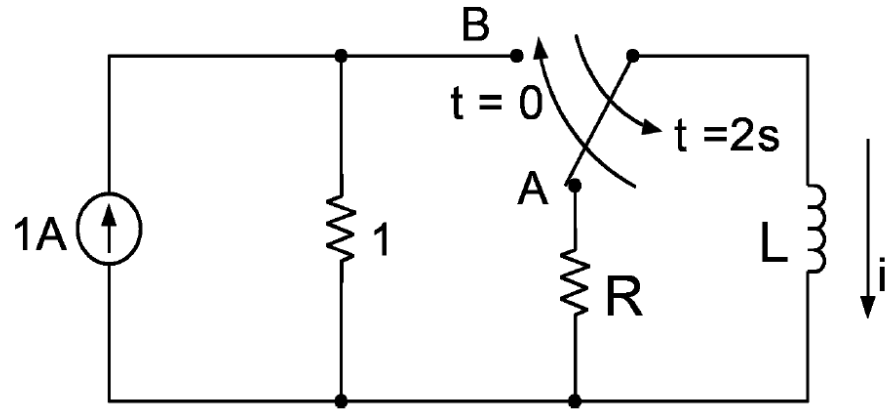2. Assume the switch has been in position A for a long time. It then moves to position B at time $t = 0$ s, and back to position A at time $t = 2$ s. Find values L and R such that $i(t) = (1 - e^{-1})$ A at $t = 2$ s, and $i(t) = (1 - e^{-1}) e^{-1}$ A at $t = 6$ s.



3. The circuit shown below has been in DC steady-state before the switch opens at $t = 0$ s. Find and sketch $v_R(t)$, $v_C(t)$, and $i_C(t)$.

